

## 20.12 CAPACITORS IN SERIES AND PARALLEL

Figure 20.36 shows two different capacitors connected in parallel to a battery. Since the capacitors are in parallel, they have the same voltage  $V$  across their plates. However, the capacitors *contain different amounts of charge*. The charge stored by a capacitor is  $q = CV$  (Equation 19.8), so  $q_1 = C_1V$  and  $q_2 = C_2V$ .

As with resistors, it is always possible to replace a parallel combination of capacitors with an *equivalent capacitor* that stores the same charge and energy for a given voltage as the combination does. To determine the equivalent capacitance  $C_P$ , note that the total charge  $q$  stored by the two capacitors is

$$q = q_1 + q_2 = C_1V + C_2V = (C_1 + C_2)V = C_PV$$

This result indicates that two capacitors in parallel can be replaced by an equivalent capacitor whose capacitance is  $C_P = C_1 + C_2$ . For any number of capacitors in parallel, the equivalent capacitance is

$$\text{Parallel capacitors} \quad C_P = C_1 + C_2 + C_3 + \dots \quad (20.18)$$


Capacitances in parallel simply add together to give an equivalent capacitance. This behavior contrasts with that of resistors in parallel, which combine as reciprocals, according to Equation 20.17.

The equivalent capacitor not only stores the same amount of charge as the parallel combination of capacitors, but also stores the same amount of energy. For instance, the energy stored in a single capacitor is  $\frac{1}{2}CV^2$  (Equation 19.11), so the total energy stored by two capacitors in parallel is

$$\text{Total energy} = \frac{1}{2}C_1V^2 + \frac{1}{2}C_2V^2 = \frac{1}{2}(C_1 + C_2)V^2 = \frac{1}{2}C_PV^2$$


which is equal to the energy stored in the equivalent capacitor  $C_P$ .

When capacitors are connected in series, the equivalent capacitance is different than when they are in parallel. As an example, Figure 20.37 shows two capacitors in series and reveals the following important fact: *All capacitors in series, regardless of their capacitances, contain charges of the same magnitude,  $+q$  and  $-q$ , on their plates*. The battery places a charge of  $+q$  on plate  $a$  of capacitor  $C_1$ , and this charge induces a charge of  $+q$  to depart from the opposite plate  $a'$ , leaving behind a charge  $-q$ . The  $+q$  charge that leaves plate  $a'$  is deposited on plate  $b$  of ca-

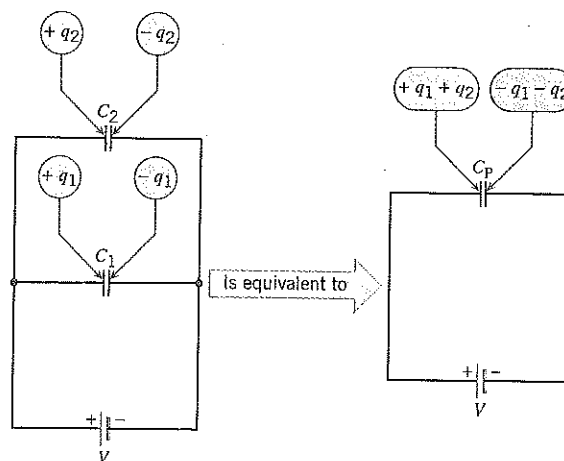

**Figure 20.36** In a parallel combination of capacitances  $C_1$  and  $C_2$ , the voltage  $V$  across each capacitor is the same, but the charges  $q_1$  and  $q_2$  on each capacitor are different.

**Figure 20.37** In a series combination of capacitances  $C_1$  and  $C_2$ , the same amount of charge  $q$  is on the plates of each capacitor, but the voltages  $V_1$  and  $V_2$  across each capacitor are different.

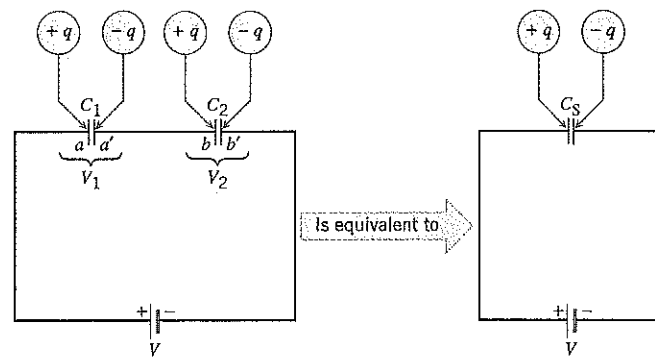

capacitor  $C_2$  (since these two plates are connected by a wire), where it induces a  $+q$  charge to move away from the opposite plate  $b'$ , leaving behind a charge of  $-q$ . Thus, all capacitors in series contain charges of the same magnitude on their plates. Note the difference between charging capacitors in parallel and in series. When charging parallel capacitors, the battery moves a charge  $q$  that is the sum of the charges moved for each of the capacitors:  $q = q_1 + q_2 + q_3 + \dots$ . In contrast, when charging a series combination of  $n$  capacitors, the battery only moves a charge  $q$ , not  $nq$ , because the charge  $q$  passes by induction from one capacitor directly to the next one in line.

The equivalent capacitance  $C_S$  for the series connection in Figure 20.37 can be determined by observing that the battery voltage  $V$  is shared by the two capacitors. The drawing indicates that the voltages across  $C_1$  and  $C_2$  are  $V_1$  and  $V_2$ , so that  $V = V_1 + V_2$ . Since the voltages across the capacitors are  $V_1 = q/C_1$  and  $V_2 = q/C_2$ , we find that

$$V = V_1 + V_2 = \frac{q}{C_1} + \frac{q}{C_2} = q \left( \frac{1}{C_1} + \frac{1}{C_2} \right) = q \left( \frac{1}{C_S} \right)$$

Thus, two capacitors in series can be replaced by an equivalent capacitor whose capacitance  $C_S$  can be obtained from  $1/C_S = 1/C_1 + 1/C_2$ . For any number of capacitors connected in series the equivalent capacitance is given by



$$\text{Series capacitors} \quad \frac{1}{C_S} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots \quad (20.19)$$

Equation 20.19 indicates that capacitances in series combine as reciprocals and do not simply add together as resistors in series do. It is left as an exercise (problem 91) to show that the equivalent series capacitance stores the same electrostatic energy as the sum of the energies of the individual capacitors.

It is possible to simplify circuits containing a number of capacitors in the same general fashion as that outlined for resistors in Example 11 and Figure 20.23. The capacitors in a parallel grouping can be combined according to Equation 20.18, and those in a series grouping can be combined according to Equation 20.19.

## 20.13 RC CIRCUITS

Many electric circuits contain both resistors and capacitors. Figure 20.38 illustrates an example of a resistor–capacitor or RC circuit. Part *a* of the drawing shows the circuit at a time  $t$  after the switch has been closed and the battery

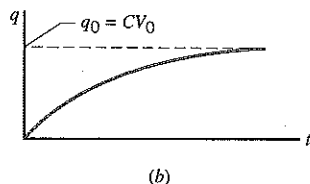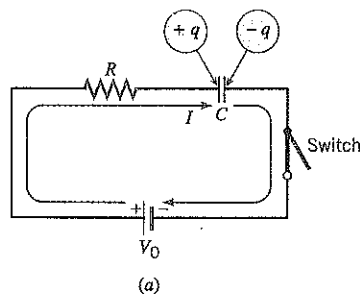

**Figure 20.38** Charging a capacitor.