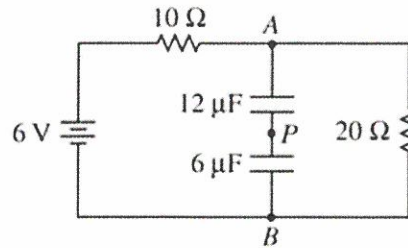


## Electric Circuits Exam Review

**Directions** – Complete the following problems to help prepare you for the upcoming test.

### 2003 AP<sup>®</sup> PHYSICS B FREE-RESPONSE QUESTIONS



2. (15 points)

A circuit contains two resistors ( $10\ \Omega$  and  $20\ \Omega$ ) and two capacitors ( $12\ \mu\text{F}$  and  $6\ \mu\text{F}$ ) connected to a  $6\ \text{V}$  battery, as shown in the diagram above. The circuit has been connected for a long time.

- Calculate the total capacitance of the circuit.
- Calculate the current in the  $10\ \Omega$  resistor.
- Calculate the potential difference between points  $A$  and  $B$ .
- Calculate the charge stored on one plate of the  $6\ \mu\text{F}$  capacitor.
- The wire is cut at point  $P$ . Will the potential difference between points  $A$  and  $B$  increase, decrease, or remain the same?

\_\_\_\_\_ increase

\_\_\_\_\_ decrease

\_\_\_\_\_ remain the same

Justify your answer.

$$\begin{aligned} \text{a) } \frac{1}{C_3} &= \frac{1}{C_1} + \frac{1}{C_2} \\ &= \frac{1}{12\ \mu\text{F}} + \frac{1}{6\ \mu\text{F}} \\ C_3 &= 4\ \mu\text{F} \end{aligned}$$

$$\begin{aligned} \text{d) } Q_T &= Q_1 = Q_2 \\ Q &= C_T V_T \\ &= (4 \times 10^{-6}\ \text{F})(4\ \text{V}) \\ &= 16 \times 10^{-6}\ \text{C} \\ &= 1.6 \times 10^{-5}\ \text{C} \end{aligned}$$

*ratio of  $V_1:V_2$   
2:1  
sum to 4*

$$\begin{aligned} Q_2 &= C_2 V_2 \\ &= (6 \times 10^{-6}\ \text{F})(2.7) \\ &= 16 \times 10^{-6}\ \text{C} \\ &= 1.6 \times 10^{-5}\ \text{C} \end{aligned}$$

$$\begin{aligned} \text{b) } \textcircled{1} R_T &= R_1 + R_2 \\ &= 10\ \Omega + 20\ \Omega \\ &= 30\ \Omega \end{aligned}$$

$$\begin{aligned} \textcircled{2} I_T &= I_1 = I_2 = \frac{V_T}{R_T} \\ &= \frac{6\ \text{V}}{30\ \Omega} \\ &= .20\ \text{A} \end{aligned}$$

$$\begin{aligned} \text{c) } V_2 &= I_2 R_2 = (.20\ \text{A})(20\ \Omega) \\ &= 4\ \text{V} \end{aligned}$$

$$V_{AB} \parallel \text{ to } V_2 = 4\ \text{V}$$

e) no current is flowing  
 $A \rightarrow B$  anyways. cutting  
the wire will not affect  
the outer loop keeping  
potential difference in  
the  $20\ \Omega$  resistor the same

## 2002 AP<sup>®</sup> PHYSICS B FREE-RESPONSE QUESTIONS

3. (15 points)

Two lightbulbs, one rated 30 W at 120 V and another rated 40 W at 120 V, are arranged in two different circuits.

- (a) The two bulbs are first connected in parallel to a 120 V source.
- i. Determine the resistance of the bulb rated 30 W and the current in it when it is connected in this circuit.
  - ii. Determine the resistance of the bulb rated 40 W and the current in it when it is connected in this circuit.
- (b) The bulbs are now connected in series with each other and a 120 V source.
- i. Determine the resistance of the bulb rated 30 W and the current in it when it is connected in this circuit.
  - ii. Determine the resistance of the bulb rated 40 W and the current in it when it is connected in this circuit.

(c) In the spaces below, number the bulbs in each situation described, in order of their brightness.

(1 = brightest, 4 = dimmest)

2 30 W bulb in the parallel circuit

1 40 W bulb in the parallel circuit

3 30 W bulb in the series circuit

4 40 W bulb in the series circuit

*parallel better → more current is more brightness P=IV  
same V  
↑P ↑I*

*P=I<sup>2</sup>R same I  
↑P ↑R*

(d) Calculate the total power dissipated by the two bulbs in each of the following cases.

i. The parallel circuit

ii. The series circuit

*b) i) R<sub>1</sub> stays same*

$$R_1 = 480 \Omega$$

$$I_T = I_1 = I_2 = \frac{V_T}{R_T} = \frac{V_T}{R_1 + R_2}$$

$$= \frac{120V}{(480\Omega + 360\Omega)}$$

$$= .14 A$$

$$a) i) R_1 = \frac{V^2}{P} = \frac{(120V)^2}{30W}$$

$$= 480 \Omega$$

$$I_1 = V_1 / R_1 = (120V) / (480\Omega)$$

$$= .25 A$$

$$ii) R_2 = \frac{V^2}{P} = \frac{(120V)^2}{40W}$$

$$= 360 \Omega$$

$$I_2 = V_2 / R_2 = (120V) / (360\Omega)$$

$$= .33 A$$

$$ii) R_2 = 360 \Omega$$

$$I_T = I_1 = I_2 = .14 A$$

$$d) i) P_T = P_1 + P_2 = 30W + 40W = 70W$$

$$ii) P_T = \frac{V^2}{R_T} = \frac{V^2}{R_1 + R_2} = \frac{(120V)^2}{480\Omega + 360\Omega} = 17W$$