

HW #1

p 613 MC 1

C 18, 19

p 614 Problems 3, 11, 49


Online - ~~Stretchable R~~

- Resistance & resistivity

(1)

p 613 - Multiple Choice

(8)

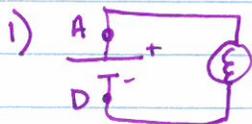

What say about current?

The current is the same at
all points in circuit

- Concept

18) Resistor connected to battery

A) How can you measure electric current in R?

• Take ammeter & connect in series
to the R

(1) B) How can you measure potential diff?

• Take voltmeter & connect in //
to the R

C) How determine R?

• Connect (A) in series, the (V) in //
Divide (V) by (A) gives R

19) A) What does it mean if current is 4A?

• There are 4C of electric charge passing through wire in each sec

B) What does it mean if pot. diff is 6V?

• One needs to do 6J of work to push 1C of charge through R

C) What does it mean if R is 5Ω ?

• The ratio of potential diff to current is 5

p 614 - Problems

3) flashlight battery

$$I = .50 \text{ A}$$

$$t = 3 \text{ h} = 10,800 \text{ s}$$

electrons = ?

$$\textcircled{1} q = It = (.50 \text{ A})(10,800 \text{ s}) = 5,400 \text{ C}$$

$$\textcircled{2} 5400 \text{ C} \left(\frac{1e}{1.60 \times 10^{-19} \text{ C}} \right)$$

$$3.38 \times 10^{22} e$$

①

11) person touch 120 V line

$$\begin{aligned} \text{a) } I = ? \text{ dry hands} \\ R = 100,000 \Omega \end{aligned}$$

$$I_{\text{dry}} = V/R = \frac{120 \text{ V}}{100,000 \Omega} =$$

$$1.2 \times 10^{-3} \text{ A} \\ (1.2 \text{ mA})$$

(2)

$$\begin{aligned} \text{b) } I = ? \text{ Wet hands} \\ R = 5000 \Omega \end{aligned}$$

$$I_{\text{wet}} = V/R = \frac{120 \text{ V}}{5000 \Omega}$$

$$.024 \text{ A} \quad (24 \text{ mA})$$

c) If current exceeds 10 mA muscles won't release

• There's no danger w/ dry hands + unsafe w/ wet hands

$$49) d = .10 \text{ mm so } r = .05 \times 10^{-3} \text{ m}$$

$$l = ?$$

$$R = 25 \Omega$$

$$\rho = 1.0 \times 10^{-7} \Omega \text{ m}$$

$$R = \frac{\rho L}{A}$$

$$L = \frac{R \cdot A}{\rho} = \frac{R \pi r^2}{\rho}$$

$$= \frac{(25 \Omega) \pi (.05 \times 10^{-3} \text{ m})^2}{1.0 \times 10^{-7} \Omega \text{ m}}$$

$$= 1.96 \text{ m}$$

(1)

- Online - Resistance + Resistivity

At same temp two wires made of pure copper have different R . The same voltage is applied at ends of each wire. The wires may differ in

(1)

- length
- cross-sectional area
- amount of current
- ~~resistivity~~