

HW 7/6

p 573 Reading 66, 67, 68, 69
WS #7 questions

p 573 - Reading

(4) Plus WS #7 actual grade

• electric eels

66) $C = 1.0 \text{ F}$
 $V = .10 \text{ V}$
 $q = ?$

$$C = q/V$$

$$q = CV$$
$$= (1.0 \text{ F})(.10 \text{ V})$$
$$= .1 \text{ C}$$



Place two 1.0 F capacitors in series


• net pot diff?

$$V_{\text{net}} = V_1 + V_2$$
$$= .1 \text{ V} + .1 \text{ V}$$
$$= .2 \text{ V}$$

(4)

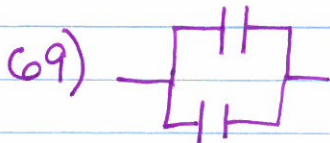68) Discharge two capacitors, how much q ?

series $Q_T = Q_1 = Q_2 = .1 \text{ C}$ (same as single)



Place two 1.0 F capacitors in parallel, net pot diff

$$V_T = V_1 = V_2 = .10 \text{ V}$$

Already graded

- Read the textbook section regarding Capacitors in Circuits from Mrs. Nadworny's webpage.
- In Mastering Physics, complete the Reading Passage questions.
- Complete the following questions. Show all work. If you need more room, attach looseleaf.

~~(5)~~
(5)

1. A $4.0 \mu\text{F}$ and an $8.0 \mu\text{F}$ capacitor are connected in parallel across a 25 V battery. Find (a) the equivalent capacitance and (b) the total charge stored in the two capacitors.

a) $C_{\text{eq}} = ?$ $C_{\text{eq}} = C_1 + C_2 = 4 \mu\text{F} + 8 \mu\text{F} = 12 \mu\text{F}$ (4)

b) $q_{\text{tot}} = ?$ $q = CV = (12 \times 10^{-6} \text{ F})(25 \text{ V}) = 3.0 \times 10^{-4} \text{ C}$ (4)

$C_1 = 4 \mu\text{F}$
 $C_2 = 8 \mu\text{F}$
 parallel
 $V_T = 25 \text{ V}$
 (1)

2. Three capacitors (4.0 , 6.0 , and $12.0 \mu\text{F}$) are connected in series across a 50.0 V battery. Find the voltage across the $4.0 \mu\text{F}$ capacitor.

$C_1 = 4.0 \mu\text{F}$
 $C_2 = 6.0 \mu\text{F}$
 $C_3 = 12.0 \mu\text{F}$
 $V_T = 50.0 \text{ V}$
 series
 $V_1 = ?$ (2)

① $C_{\text{eq}} = \left(\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right)^{-1} = \left(\frac{1}{4 \mu\text{F}} + \frac{1}{6 \mu\text{F}} + \frac{1}{12 \mu\text{F}} \right)^{-1} = 2 \mu\text{F}$ (2)

② $Q_T = Q_1 = Q_2 = Q_3$
 $Q = CV = (2 \times 10^{-6} \text{ F})(50.0 \text{ V}) = 1.0 \times 10^{-4} \text{ C}$ (2)

③ $V_1 = \frac{Q}{C} = \frac{1.0 \times 10^{-4} \text{ C}}{4.0 \times 10^{-6} \text{ F}} = 25 \text{ V}$ (2)

3. A $3.0 \mu\text{F}$ capacitor and a $4.0 \mu\text{F}$ capacitor are connected in series across a 40.0 V battery. A $10.0 \mu\text{F}$ capacitor is also connected directly across the battery terminals. Find the total charge that the battery delivers to the capacitors.

$C_1 = 3.0 \mu\text{F}$
 $C_2 = 4.0 \mu\text{F}$ series w/ $V_T = 40 \text{ V}$
 $C_3 = 10.0 \mu\text{F}$ parallel w/ battery (2)
 $Q_T = ?$

① series: $C_{1,2} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1} = \left(\frac{1}{3 \mu\text{F}} + \frac{1}{4 \mu\text{F}} \right)^{-1} = 1.7 \mu\text{F}$ (2)

② $C_{\text{Tot}} = C_{1,2} + C_3 = 1.7 \mu\text{F} + 10 \mu\text{F} = 11.7 \mu\text{F}$ (2)

③ $Q_T = C_T V_T = (11.7 \times 10^{-6} \text{ F})(40 \text{ V}) = 4.7 \times 10^{-4} \text{ C}$ (2)