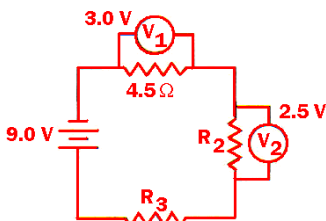


### Circuits Review

**Directions:** Solve the following problems using the GUESS method and proper significant figures. Be sure to show ALL work.

1. A circuit contains three resistors ( $R_1$  is 4.5 ohms,  $R_2$  and  $R_3$  are unknown) in series with a 9.0 volt battery. A voltmeter attached to  $R_1$  reads 3.0 volts. A voltmeter attached to  $R_2$  reads 2.5 volts.
  - a. Draw a circuit schematic of the circuit detailed above. Remember to use proper schematic symbols and label it.



- b. Calculate the potential drop across resistor  $R_3$ .

$$\begin{aligned}
 V &= V_1 + V_2 + V_3 \\
 V_3 &= V - (V_1 + V_2) \\
 &= 9.0V - (3.0V + 2.5V) \\
 &= 3.5V
 \end{aligned}$$

- c. Calculate the current that passes through  $R_1$ .

$$I = \frac{V_1}{R_1} = \frac{3.0V}{4.5\Omega} = 0.67A$$

- d. Determine the current that passes through  $R_2$  and  $R_3$ .

$$I_T = I_1 = I_2 = I_3 = 0.67A$$

- e. Calculate the resistances of  $R_2$  and  $R_3$ .

$$R_2 = \frac{V_2}{I_2} = \frac{2.5V}{0.67A} = 3.7\Omega \quad R_3 = \frac{V_3}{I_3} = \frac{3.5V}{0.67A} = 5.2\Omega$$

- f. Calculate the equivalent resistance of the circuit.

$$R_{eq} = R_1 + R_2 + R_3 = 4.5\Omega + 3.7\Omega + 5.2\Omega = 13.4\Omega$$


2. How many charges flow through a circuit if a 24 A current is allowed to flow for 2.7 minutes?

$$q = It = 24A (162s) = 3900C \left( \frac{1e}{1.60 \times 10^{-19}C} \right) = 2.4 \times 10^{22} e$$

3. When a 43  $\Omega$  resistor is connected to a battery, the current in the circuit is 0.54 A. What is the voltage of the battery?

$$V = IR = 0.54A(43\Omega) = 23V$$

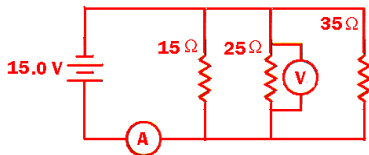4. A circuit contains three resistors ( $R_1$  is 15 ohms,  $R_2$  is 25 ohms, and  $R_3$  is 35 ohms) in parallel with a 15.0 volt battery.
- Draw a circuit schematic of the circuit detailed above. Remember to use proper schematic symbols and label it. Also include an ammeter capable of reading the total current in the circuit and a voltmeter capable of reading the potential difference across the 25 ohm resistor.



- Determine the potential difference across each resistor.

$$V = V_1 = V_2 = V_3 = 15.0V$$

- Calculate the current flowing through each resistor.

$$I_1 = \frac{V_1}{R_1} = \frac{15.0V}{15\Omega} = 1.0A$$

$$I_2 = \frac{V_2}{R_2} = \frac{15.0V}{25\Omega} = 0.60A$$

$$I_3 = \frac{V_3}{R_3} = \frac{15.0V}{35\Omega} = 0.43A$$

- Calculate the total current flowing through the circuit.

$$I = I_1 + I_2 + I_3 = 1.0A + 0.60A + 0.43A = 2.0A$$

- Calculate the equivalent resistance of the circuit.

$$R_T = \frac{V_T}{I_T} = \frac{15.0V}{2.0A} = 7.5\Omega$$

or

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} = \frac{1}{15\Omega} + \frac{1}{25\Omega} + \frac{1}{35\Omega} = \frac{35}{525\Omega} + \frac{21}{525\Omega} + \frac{15}{525\Omega} +$$

$$\frac{1}{R} = \frac{71}{525\Omega}$$

$$R = 7.4\Omega$$

5. A tungsten wire that is 4.0 meters long with a diameter of 2.6 mm at 20°C. It is part of a circuit connected to a 7.5 volt battery.

- Calculate the resistance of the wire.

$$R = \frac{\rho L}{A} = \frac{\rho L}{\pi r^2} = \frac{(5.60 \times 10^{-8} \Omega \cdot m)(4.0m)}{\pi (.0013m)^2} = .042\Omega$$

- Calculate the current in the wire.

$$I = \frac{V}{R} = \frac{7.5V}{.042\Omega} = 180A$$

Any of the three will work!

- Calculate the power used by the circuit.

$$P = IV = (180A)(7.5V) = 1400W \quad P = I^2R = (180A)^2(0.042\Omega) = 1400W \quad P = \frac{V^2}{R} = \frac{(7.5V)^2}{0.042\Omega} = 1300W$$

- Calculate the energy required to power the circuit if it runs for 4.5 minutes.

$$W = Pt = (1400W)(270s) = 3.8 \times 10^5 J$$

$$W = Pt = (1300W)(270s) = 3.5 \times 10^5 J$$