

Name _____
Honors Physics
Period _____







Date _____
Electric Circuits WS #4H
Mrs. Nadworny





Electrical Power & Energy

Directions: Read online textbook pages 708 – 713. Solve the following problems using the GUESS method and proper significant figures. Be sure to show ALL work.

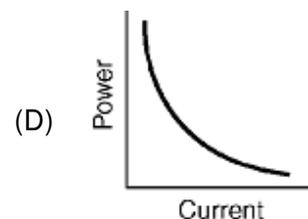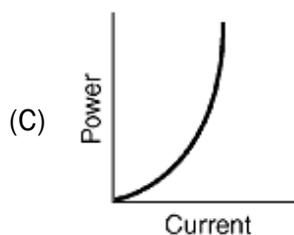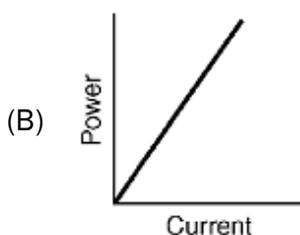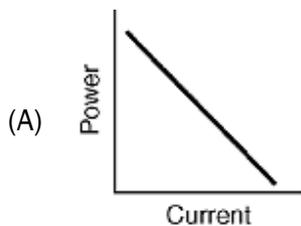- As the potential difference across a given resistor is increased, the power expended in moving charge through the resistor
(A) increases (B) decreases (C) remains the same
- One watt is equivalent to one
(A) $N \cdot m$ (B) $J \cdot s$ (C) N/m (D) J/s
- Which graph best represents the relationship between the electrical power and the current in a resistor that obeys Ohm's Law



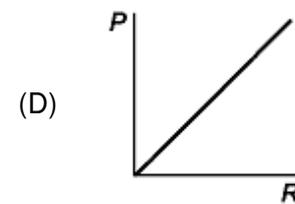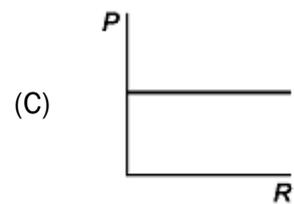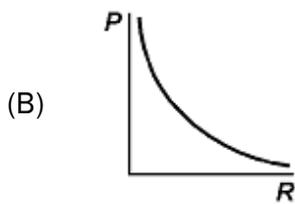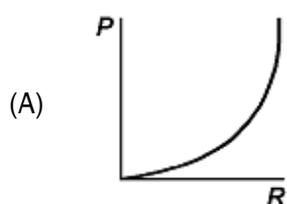- The potential difference applied to a circuit element remains constant as the resistance of the element is varied. Which graph best represents the relationship between power (P) and resistance (R) of this element?



- An electric doorbell provides 2.3 ohms of resistance in a circuit. The current through the doorbell is 1.8 A.
 - What is the power rating of the doorbell?

 - How much electric energy does the doorbell convert in 1.5 seconds?

Continued on next page

